

Roll No.

TEE-101

**B. TECH. (FIRST SEMESTER)
END SEMESTER EXAMINATION, 2019**

(All Branches)

BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

1. Attempt any *two* parts of choice from (a), (b) and (c). (10×2=20 Marks)

(a) State and explain the Superposition Theorem with suitable example along with its limitations. (CO1)

(b) Determine the Thevenin's Equivalent for the circuit as shown in Fig. 1. : (CO1)

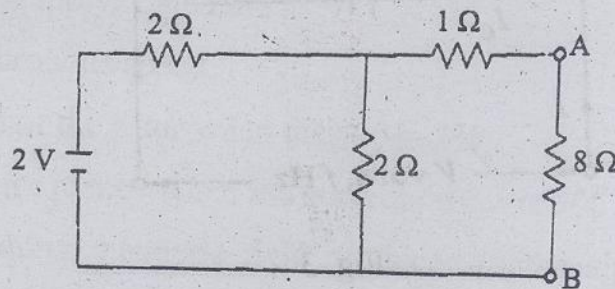


Fig. 1

(c) Calculate the value of current in branch AB, in circuit as shown in Fig. 2, using Node analysis : (CO1)

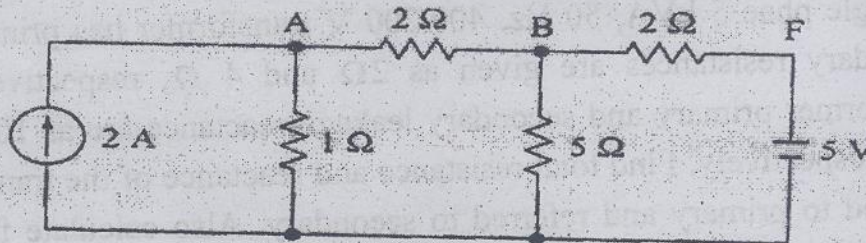


Fig. 2

2. Attempt any *two* parts of choice from (a), (b) and (c). (10×2=20 Marks)
- (a) Derive the relation between line quantities and phase quantities for 3-phase delta connection. (CO3)
- (b) A coil of inductance 0.08 H and negligible resistance is connected in series with $15\ \Omega$ non-inductive resistance. The combined circuit is energized from a 240 V, 50 Hz supply. Calculate : (CO2)
- Reactance of the coil
 - Impedance of the circuit
 - The current in the circuit
- (c) What do you mean by electrical resonance ? Derive the condition of resonance as shown in the Fig. 3 given below : (CO2)

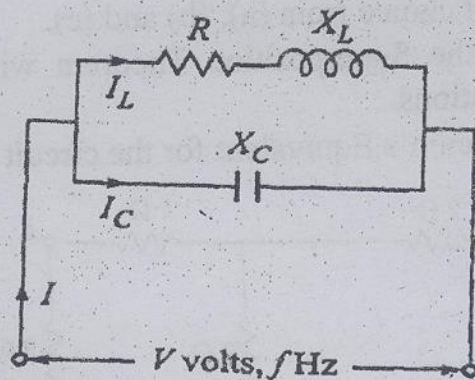


Fig. 3

3. Attempt any *two* parts of choice from (a), (b) and (c). (10×2=20 Marks)
- (a) Write similarities and dissimilarities between electrical and magnetic circuit. (CO4)
- (b) A single phase 5 kVA, 50 Hz, 400/200 V transformer has primary and secondary resistances are given as $2\ \Omega$ and $4\ \Omega$, respectively, and transformer primary and secondary leakage reactance are as $10\ \Omega$ and $5\ \Omega$, respectively. Find total resistance and reactance of the transformer referred to primary and referred to secondary. Also calculate full load and half load copper loss. (CO4)

(3)

- (c) Discuss the various characteristics of an ideal transformer. Also, draw equivalent circuit of practical transformer and discuss its various electrical parameters. (CO4)

4. Attempt any *two* parts of choice from (a), (b) and (c). (10×2=20 Marks)

(a) Write short notes on the following : (CO5)

(i) MCB

(ii) ELCB

(b) What is Lead Acid Battery ? Explain along with its advantages and disadvantages. (CO5)

(c) What is the need of power factor improvement ? Explain any *one* method for power factor improvement. (CO5)

5. Attempt any *two* parts of choice from (a), (b) and (c). (10×2=20 Marks)

(a) Write and explain the working principles of DC generator. (CO6)

(b) A three phase Induction motor is wound for four poles and is supplied from a 50 Hz supply. Calculate : (CO6)

(i) the synchronous speed

(ii) the speed of the rotor when the slip is 3%

(iii) the rotor frequency when the speed of rotor is 900 rpm

(c) How is a rotating magnetic field produced in the air gap of 3-phase induction motor ? (CO6)