

Roll No. ....

## TEE-101

### B. TECH. (FIRST SEMESTER) MID SEMESTER EXAMINATION, 2018

(All Branches)

BASIC ELECTRICAL ENGINEERING

Time : 1:30 Hours

Maximum Marks : 50

**Note :**(i) This question paper contains two Sections.

(ii) Both Sections are compulsory.

#### Section—A

1. Fill in the blanks/True-False : (1×5=5 Marks)

(a) The resistance of an ideal voltage source is .....

(b) The value of peak factor for an AC sinusoidal waveform is .....

(c) In three-phase AC star delta networks, line voltage is equal to phase voltage.

(True/False)

(d) Resonance does not occur due to LC components in circuits. (True/False)

(e) Thevenin's voltage is also known as open circuit voltage. (True/False)



(2)

TEE-101

2. Attempt any *five* parts : (3×5=15 Marks)

- Define Kirchoff's current law.
- Distinguish between ideal and practical electrical energy source.
- Define Norton's theorem.
- Define power factor and mention its significance in electric networks.
- Define RMS value of an AC signal.
- Define line and phase voltage in three-phase AC circuits.

**Section—B**3. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)

- State and explain Superposition theorem.
- Calculate the current through  $4\ \Omega$  resistance in the given network using Superposition theorem (Refer Figure 1).

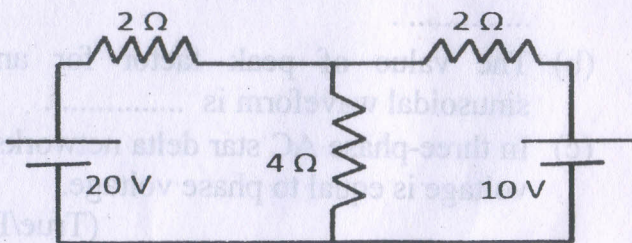


Fig. 1

(3)

TEE-101

- Explain mesh analysis. Find the current  $I$  for the given electrical circuit (Figure 2) using mesh analysis.

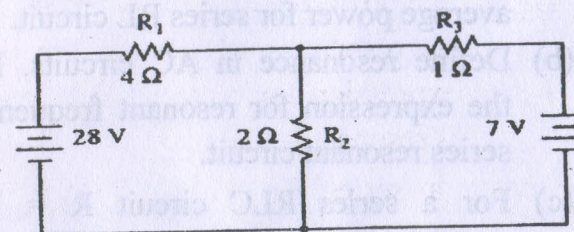


Fig. 2

4. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)

- Find the Thevenin equivalent circuit across  $10\ \Omega$  resistance as shown in Figure 3 and hence find load current  $I_L$ .

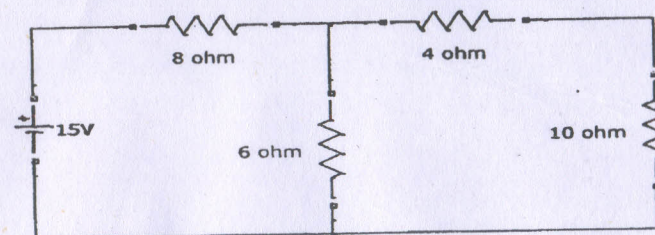


Fig. 3

- Explain nodal analysis with suitable example.
- Derive expression for line and phase values of voltage and current for 3-phase delta connected balanced load system.



5. Attempt any two parts of choice from (a), (b) and (c). (5×2=10 Marks)

- (a) Obtain an expression for instantaneous and average power for series RL circuit.
- (b) Define resonance in AC circuits. Derive the expression for resonant frequency for series resonant circuit.
- (c) For a series RLC circuit  $R = 10 \Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = 8 \mu\text{F}$ . Determine value of resonant frequency.

