

Roll No.

TEE-101

**B. TECH. (FIRST SEMESTER)
MID SEMESTER EXAMINATION, 2019
(ALL BRANCHES)
BASIC ELECTRICAL ENGINEERING**

Time : 1 : 30 Hours

Maximum. Marks : 50

Note : (i) All questions are compulsory.

(ii)- Answer **any two** subquestions among (a), (b) and (c) in each main question.

(iii) Total marks for each main question are ten.

1. Attempt any *two* parts of choice from (a), (b) and (c). (2x5=10 Marks)

(a) State and explain the following laws with suitable example


(i) Ohm's law

(ii) **Kirchhoff's** current law

(iii) Kirchhoffs voltage law

• TEE-101

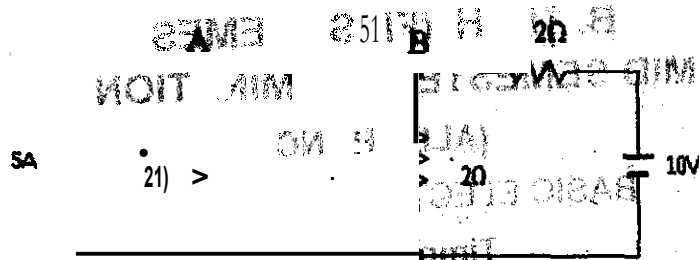- (b) Find current in each branch of electrical circuit, as shown in Fig. 2, using voltage method.



- (c) Find current in each branch, shown in Fig. 2, using mesh analysis. All resistances, as indicated in Fig 2, are in

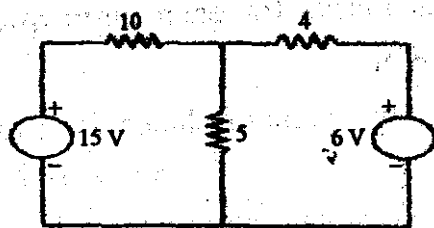


Fig. 2

2. Attempt any two parts of choice from (a), (b) and (c). (2x 5=10 Marks)
- (a) State and explain **Thevenin's** theorem with suitable circuit diagram.

3)

TEE-101

- (b) Using **Thevenin's** theorem, calculate current in branch AB, as shown in Fig. 3. All resistance are in Ω .

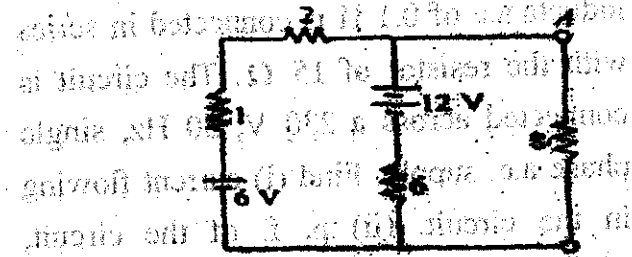


Fig. 3

- (c) Find current, I_1 and I_2 as shown in Fig. 4, using mesh analysis.

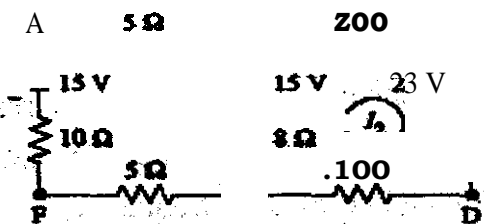


Fig. 4

3. Attempt any two parts of choice from (a), (b) and (c). (2x5=10 Marks)

(a) Discuss the following terms :

- IL M. S. value of AC
- Average value of AC
- Form factor
- Peak factor

(4)

TEE-101

- (b) Determine the M. S. value of **full wave** rectified current which is obtained from sinusoidal AC with time period T.
- (c) A reactor having negligible resistance and inductance of 0.1 H is connected in series with the resistor of $15\ \Omega$. The circuit is connected across a 230 V, 50 Hz, single phase a.c. supply. **Find (i)** current flowing in the circuit, **(ii)** p. f. of the circuit, **(iii)** active power **(iv)** reactive power.

4. Attempt any *two* parts of choice from (a), (b) and (c).
(2x5=10 Marks)

(a) Discuss **phenomenon of electrical resonance** in circuit having resistance, capacitance and inductance in series. Also, calculate resonance frequency.

(b) A circuit having a resistance of $5\ \Omega$, an inductance of 0.4 H and a variable capacitance in series, is connected across a 110 V, 50 Hz supply. Calculate (i) the value of capacitance to give resonance, (ii) current under the condition of

(5)

TEE-101

resonance; (iii) voltage across the inductance under the resonance condition.

(c) **Derive the** relation between line and phase voltage in three-phase star-connected balanced system.

5 Attempt any *two* parts of choice from (a), (b) and (c).
(2x5=10 Marks)

- (a) Discuss superposition theorem with suitable example,
- (b) Find current in $10\ \Omega$ resistance, as shown in Fig. 5, using Superposition theorem.

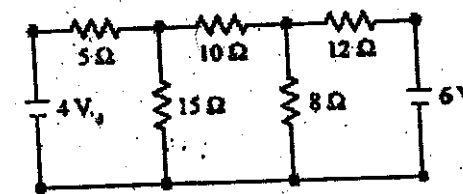


Fig. 5

- (c) An inductance of 50 mH is connected in series with a resistance of $10\ \Omega$. The voltage applied to the circuit is 200 V, 50 Hz. Calculate (i) impedance, (ii) current in the circuit (iii) p. f. of the circuit.

TEE-101