

Roll No.

TEC-101

**B. TECH. (FIRST SEMESTER)
END SEMESTER EXAMINATION, 2019**

(All Branches)

BASIC ELECTRONICS ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

1. Attempt any *two* parts of choice from (a), (b) and (c). (2×10=20 Marks)

(a) With the help of energy band diagram explain the mechanism of insulator, metal and semiconductor.

(b) Explain the contact potential in a p-n junction. An abrupt silicon p-n junction has $N_a = 1 \times 10^{16} \text{ cm}^{-3}$ on one side and $N_d = 1 \times 10^{17} \text{ cm}^{-3}$ on other side, determine its contact potential. Given $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$.

(c) With the help of suitable diagram explain the working principle of p-n junction diode. Draw its energy band diagram and also explain the mechanism drift and diffusion current component.

2. Attempt any *two* parts of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Draw and explain the circuit diagram of full wave rectifier. Also draw its peak load voltage waveform. What will happen when a capacitor is placed across the load resistance of a full wave rectifier circuit ? Explain with suitable waveform .

- (b) Fig. 1 shows a simple Zener diode voltage regulator circuit. The voltage across the load is to be maintained constant 12 V while the load current varies from 0 to 200 mA. Find the value of V_Z and R_S . Also find the maximum power rating of Zener diode :

 


Fig. 1

- (c) What do you mean by unregulated and regulated power supply ? Draw and explain the block diagram of a regulated power supply. Assume that the regulated supply produces little amount of ripple, then how it affect the performance of an audio amplifier and digital circuit.
3. Attempt any *two* parts of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain common base configuration of BJT with suitable diagram. Also draw its input and output characteristics.
- (b) A silicon BJT with $\beta = 100$, is shown in Fig. 2, compute the transistor parameters i_B , i_C , i_E and V_{CE} . In which mode the BJT is operating ?
- (c) Explain all three configurations of a BJT in terms of :
- Input impedance
 - Output impedance
 - Voltage gain
 - Current gain

 


Fig. 2

4. Attempt any *two* parts of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Explain the ideal characteristics of an op-amp in terms of input impedance, output impedance, differential and common mode voltage gain, common mode rejection ratio, slew rate. Under what condition the open loop gain become infinite?

(b) An op-amp based differential amplifier is shown in Fig. 3. Derive the expression for its output voltage (V_{out}) in terms of V_1 and V_2 . Also find the value of the output voltage, assume $V_1 = 2\text{ V}$, $V_2 = 3\text{ V}$, when $R_1 = R_2 = 1\text{ k}\Omega$, $R_3 = 5\text{ k}\Omega$, and $R_4 = 8\text{ k}\Omega$.

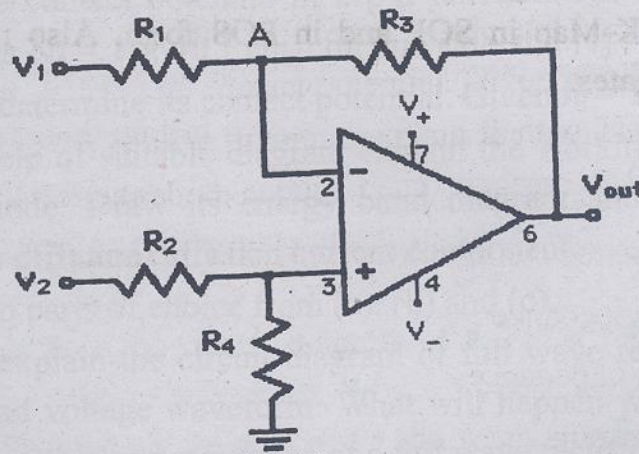


Fig. 3

- (c) Draw the circuit diagram and derive the expression for the output voltage of an op-amp based integrator. Also draw the output wave form when a square wave is applied at the input to this integrator.

5. Attempt any *two* parts of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Find the following :

(i) $(10.11)_2 = (\dots\dots\dots)_{10}$

(ii) $(6.5)_{10} = (\dots\dots\dots)_5$

(iii) $(57.32)_8 = (\dots\dots\dots)_2$

(iv) $(257)_N = (140)_{10}$, find N

(v) $(103)_8 - (45)_8 = (X)_5$, find X

(b) (i) Simply the following Boolean functions :

$$F = A \left(A + \bar{C} (\overline{AB + A\bar{C}}) \right)$$

(ii) What is the difference between canonical form and standard forms of representation of Boolean function ? Explain with suitable example.

(c) (i) Convert the following Boolean function in SOP, POS and Canonical SOP form :

$$F = (AB + C)(B + \bar{C}D)$$

(ii) Minimize the given function $F = \Sigma (0, 2, 3, 6, 7) + d(8, 10, 11, 15)$ using K-Map in SOP and in POS form. Also realize using basic logic gates.