

8909 921921

Roll No.

TEE-101

**B. TECH. (FIRST SEMESTER)
MID SEMESTER EXAMINATION, NOV., 2021**

(All Branches)

BASIC ELECTRICAL ENGINEERING

Time : 1½ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each question carries 10 marks.

1. (a) Define Kirchhoff's laws. Describe the significance of these laws in electrical circuits. 10 Marks (CO1)


OR

- (b) Define the following terms as associated with electrical circuits :


10 Marks (CO1)

- (i) Branch
- (ii) Junction
- (iii) Mesh
- (iv) Active elements
- (v) Passive elements

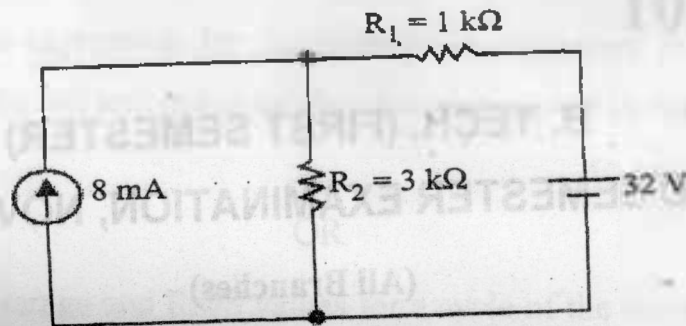
2. (a) State and explain Superposition Theorem with suitable example. Apply Superposition Theorem in the circuit given below and calculate the current through R_1 resistance. 10 Marks (CO2, CO5)



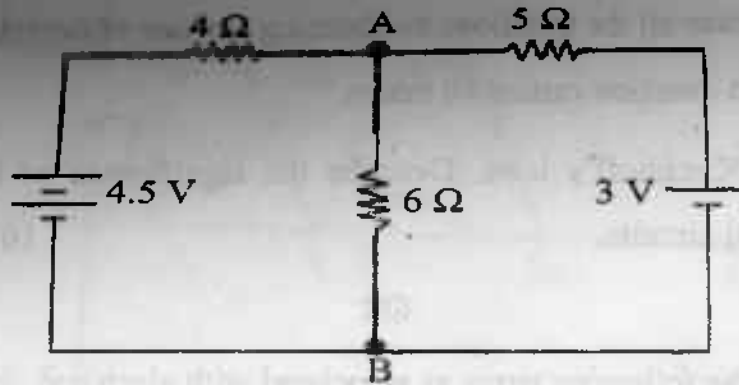- (b) Explain the procedure to solve an electrical network using Thevenin's Theorem. Find the Thevenin's voltage across A-B terminals. 10 Marks (CO2, CO5)



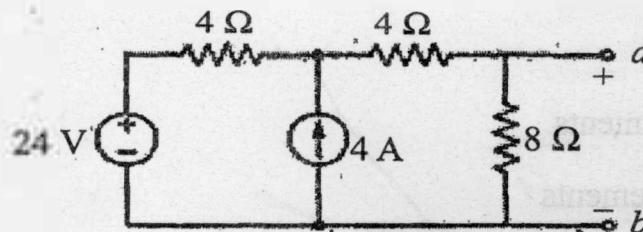3. (a) Define Norton's Theorem as used in DC circuits. Find Norton's equivalent of the circuit shown below across terminals $a-b$. 10 Marks (CO1, CO5)



(3)

TEE-101

OR

(b) What do you understand by maximum power transfer theorem ? What is the condition for the maximum power transfer in DC circuits ? Explain in brief.


10 Marks (CO1, CO5)

4. (a) Define the following terms as associated with alternating quantity :

10 Marks (CO2, CO5)

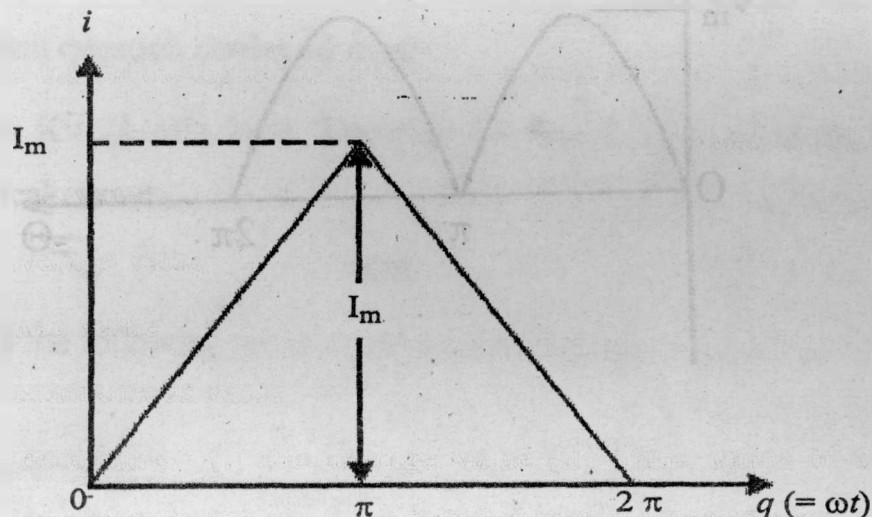- (i) Peak value
- (ii) Average value
- (iii) RMS value
- (iv) Instantaneous value

Also, determine : (i) the average value (ii) r.m.s. value of triangular wave (as shown in figure). Also find the form factor and peak factor.



OR

(b) An alternating current is given by; $i = 141.4 \sin 314t$.

Calculate :

10 Marks (CO2, CO5)

- (i) the maximum value

P. T. O.

- (ii) frequency
- (iii) time period
- (iv) the instantaneous value when $t = 3$ ms.

5. (a) Deduce an expression for the average (real) power in a single-phase series RL circuit and hence explain the term power factor.

10 Marks (CO1, CO2)

OR

(b) Find the average and RMS values for a cycle of the waveform shown in fig. below :

10 Marks (CO1, CO2)

