

Roll No.

--	--	--	--	--	--	--	--

TEE-101

B. Tech. (First Semester)

Mid Semester EXAMINATION, 2017

(All Branche)

BASIC ELECTRICAL ENGINEERING

Time : 1:30 Hours]

[Maximum Marks : 50

Note : (i) This question paper contains two Sections.

(ii) Both Sections are compulsory.

Section—A

1. Fill in the blanks/True-False : (1×5=5 Marks)

(a) The value of resistance in open circuit condition any two-terminal circuit is

(b) KCL is valid only for D.C. circuit.

(True/False)

(c) Average power of a purely inductive a. c. circuit is equal to

(d) Internal resistance of ideal voltage source is infinite. (True/False)

(e) 3 resistances of R Ω each are connected in delta. Its equivalent star will comprise resistances of value

2. Attempt any *five* parts : (3×5=15 Marks)


(Define/Short Numerical/Short Programming/Draw)

- Define bilateral and unilateral elements.
- Draw phasor diagram for series RL a. c. circuit and waveform for voltage and current.
- Define active, reactive and apparent power for a. c. circuits.
- Define Thevenin's theorem.
- Define ideal and practical current sources.
- Define the following terms :
 - frequency
 - time period
 - cycle, for a sinusoidal waveform


Section—B

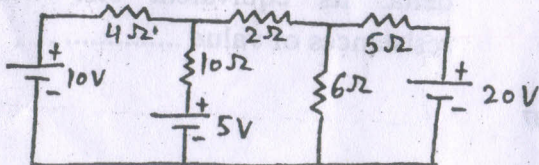3. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)

- State Maximum Power Transfer theorem for D.C. circuits. Derive the relationship for maximum power transfer condition and efficiency.
- Use Mesh analysis to find current in the 10 Ω resistance and voltage across 5 Ω resistance of the network shown below.




- Define RMS value for an a. c. circuit. Calculate the average value, r. m. s. value and form factor of output voltage wave of a half-wave rectifier, shown below.

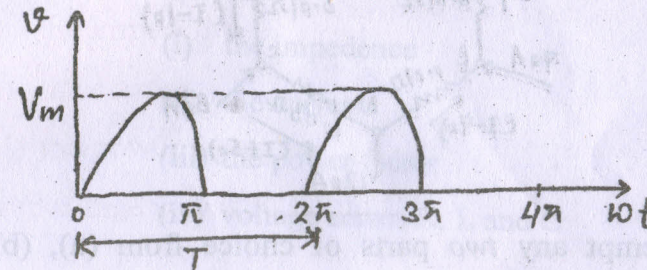

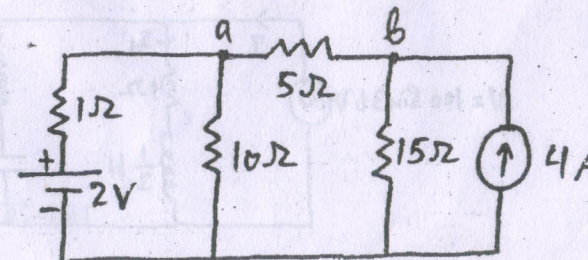4. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)


- How star to delta transformation takes place for any two-terminal network. Derive the expression.
- Use Thevenin's theorem to find the current through 5 Ω resistor in the circuit shown below.



[4]

TEE-101

- (c) Give the statement of KCL. Find the currents in all branches of the network shown below :

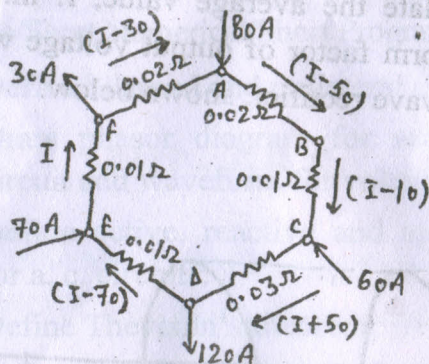


5. Attempt any *two* parts of choice from (a), (b) and (c).
(5×2=10 Marks)

(a) Explain a purely capacitive a. c. circuit with proper diagram and waveforms. Also derive the expression for average power of purely capacitive a. c. circuit.

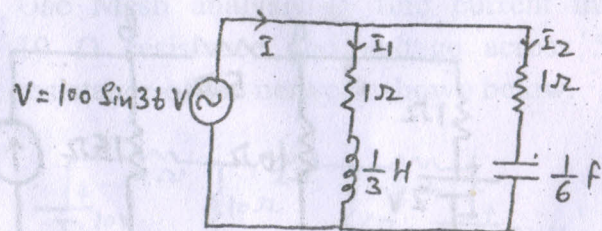(b) In the circuit shown below, a voltage $v = 100 \sin 3t$ is applied. Determine :

- Branch currents I_1 and I_2 with their phase angles.
- Total current supplied by the source and its phase angle.



[5]

TEE-101

- (c) A resistance of 15Ω , an inductance of 200 mH and a capacitance of $100 \mu\text{F}$ are connected in series A 200 V , 50 Hz , a. c. supply is connected across this series circuit. Calculate :

- the impedance
- the current
- the power factor
- voltage across R, L and C

TEE-101

400